




## Sections 3.7-3.9 Combinational Circuit Implementation

G. W. Cox – Spring 2010
   
### Bubble notation

To keep diagrams simple, we can represent the complement operation with just the circle part of the inverter gate.

Among other things, this helps us visualize ways to convert between gate types:




G. W. Cox – Spring 2010

## Review – 2-level NAND implementations

cs309

We can go directly from an SOP expression to a 2-level NAND circuit

$$f(ABC) = A'B'C + A'BC' + AB'C' + ABC$$

 

Note that a 2-level implementation does not necessarily use the minimum number of gates, nor can we constrain the number of inputs to the gates

G. W. Cox – Spring 2010


## General process for 2-level NAND circuits

cs309


1. Simplify the function into SOP form
2. Use a first-level NAND for each term that has at least 2 literals
3. Use a second-level NAND to combine all terms
4. Invert any term with one literal in the first level.

Example 3.10

$$F(xyz) = \Sigma m(1-7)$$

 

$$F(xyz) = xy' + x'y + z$$

 

Note that the term with a single literal has to be complemented.


G. W. Cox – Spring 2010

## 2-Level NOR circuits

cs309

To implement a two-level circuit using NOR gates, start with POS form

$$F(ABCDE) = (A+B)(C+D)E$$

 


G. W. Cox – Spring 2010

## AND-OR-Invert Circuits

cs309

Start with the complemented form of an SOP expression:

$$F(ABCDE) = (AB + CD + E)'$$

 


G. W. Cox – Spring 2010

## OR-AND-Invert

cs309

Start with the complemented form of the POS expression:

$$F(ABCDE) = ((A+B)(C+D)E)'$$

 


G. W. Cox – Spring 2010
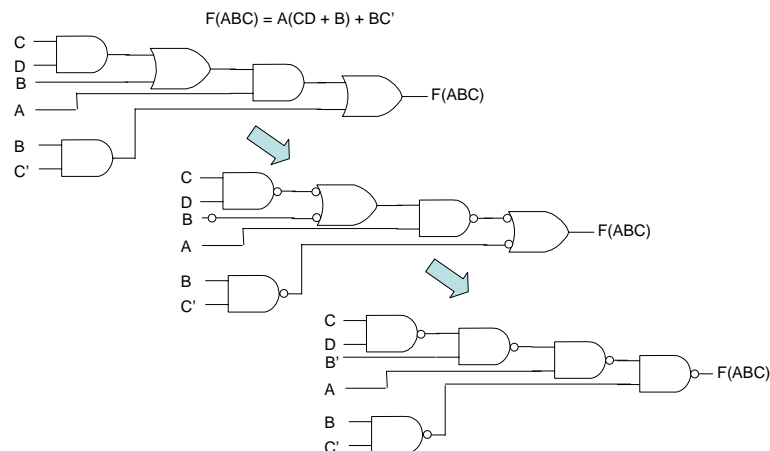
## Multi-level implementations

cs309

For a number of possible reasons (reducing # of gates, reducing # of gate inputs, producing partial results,...) you may want to have more than 2 levels.



G. W. Cox – Spring 2010

## XOR gates - review

cs309

- $A \text{ XOR } B = AB' + A'B$
- Some characteristics:
  - $x \text{ XOR } 0 = x$
  - $x \text{ XOR } 1 = x'$
  - $x \text{ XOR } x = 0$
  - $x \text{ XOR } x' = 1$
  - $x \text{ XOR } y' = x' \text{ XOR } y = (x \text{ XOR } y)'$
- XOR implements the "odd" function:
  - $a \text{ XOR } b \text{ XOR } c \text{ XOR } \dots = 1$  IFF an odd # of  $(a,b,c,\dots)$  equals 1


G. W. Cox – Spring 2010

## XORs in Parity Encoding


cs309

- Recall that we can add a "parity bit" to a data item that lets us detect some errors
  - "odd parity" == set the parity bit so that the overall # of 1's is odd
  - "even parity" == set the parity bit so that the overall # of 1's is even

Even parity generator for 3-bit data

 

Even parity checker for 3-bit data

 

G. W. Cox – Spring 2010