

Chapter 5: Synchronous Sequential Logic

G. W. Cox – Spring 2010

The idea of a sequential circuit

 


Fig. 5-1 Block Diagram of Sequential Circuit

"Next State"

"Present State"

G. W. Cox – Spring 2010

Artwork
© 2002 Prentice Hall, Inc.
M. Morris Mano
DIGITAL DESIGN, 3e.

Synchronous sequential circuits

cs309

 
 



Fig. 5-2 Synchronous Clocked Sequential Circuit

G. W. Cox – Spring 2010

Artwork
© 2002 Prentice Hall, Inc.
M. Morris Mano
DIGITAL DESIGN, 3e.

An example flip-flop

cs309

 

	Next State $Q(t+1)$	Enable	Present State $Q(t)$
	1	0	?
	1	1	1
	⋮	⋮	⋮
	whatever	0	1
	⋮	⋮	⋮
	0	0	1
	0	1	0

Time ↓

G. W. Cox – Spring 2010

Building Flip-Flops

cs309

The heart of a flip-flop is a "latch" circuit

 


Fig. 5-3 SR Latch with NOR Gates


Can also do this with NAND's – see text

Artwork
© 2002 Prentice Hall, Inc.
M. Morris Mano
DIGITAL DESIGN, 3e.

G. W. Cox – Spring 2010

How a latch holds a value


cs309

 

G. W. Cox – Spring 2010

An S-R Flip-Flop

cs309

 


C	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$; Reset state
1	1	0	$Q = 1$; set state
1	1	1	Indeterminate

(a) Logic diagram

(b) Function table

Fig. 5-5 SR Latch with Control Input

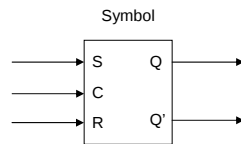

Symbol

Characteristic Table

S	R	Q(t+1)
0	0	Q(t)
0	1	0 "Reset"
1	0	1 "Set"
1	1	Not allowed


Artwork

© 2002 Prentice Hall, Inc.
M. Morris Mano
DIGITAL DESIGN, 3e.

G. W. Cox – Spring 2010

J-K Flip-Flop

cs309

 


Characteristic Table

J	K	Q(t+1)
0	0	Q(t)
0	1	0 "Reset"
1	0	1 "Set"
1	1	$Q'(t)$ "Complement"

G. W. Cox – Spring 2010

D Flip-Flop

cs309

 


Characteristic Table

D	Q(t+1)
0	0
1	1

G. W. Cox – Spring 2010

T ("Toggle") Flip-Flop

cs309

 

Characteristic Table

T	Q(t+1)
0	Q(t)
1	Q'(t)

G. W. Cox – Spring 2010

Master-Slave Flip-Flop

cs309

We often want to be able to read a stable Present State at the same time we are changing the Next State. We can do this by cascading two latches.

 


Fig. 5-9 Master-Slave D Flip-Flop

G. W. Cox – Spring 2010

Artwork
© 2002 Prentice Hall, Inc.
M. Morris Mano
DIGITAL DESIGN, 3e.

cs309

Analyzing Sequential Circuits

G. W. Cox – Spring 2010

Example Circuit

cs309

 


Fig. 5-15 Example of Sequential Circuit

G. W. Cox – Spring 2010

Note:
The "state" of this circuit
is the output of the two
flip-flops: AB

Artwork
© 2002 Prentice Hall, Inc.
M. Morris Mano
DIGITAL DESIGN, 3e.

Flip-Flop Input Equations

cs309

 


Fig. 5-15 Example of Sequential Circuit

G. W. Cox – Spring 2010

$$D_A = A(t)x(t) + B(t)x(t)$$

$$D_B = A'(t)x(t)$$

Artwork
© 2002 Prentice Hall, Inc.
M. Morris Mano
DIGITAL DESIGN, 3e.

State Equations

cs309

 


Fig. 5-15 Example of Sequential Circuit

G. W. Cox – Spring 2010

The State Equations specify the next state of the circuit as a function of the present state and inputs.

Because these are D FF's, the next state is equal to the FF inputs

$$A(t+1) = A(t)x(t) + B(t)x(t)$$

$$B(t+1) = A'(t)x(t)$$

Usually, we drop the "(t)":

$$A(t+1) = xA + xB$$

$$B(t+1) = A'x$$

Output:
 $y = (A+B)x'$

Artwork
 © 2002 Prentice Hall, Inc.
 M. Morris Mano
 DIGITAL DESIGN, 3e.

State Table

cs309

 


Fig. 5-15 Example of Sequential Circuit

G. W. Cox – Spring 2010

$$A(t+1) = xA + xB$$

$$B(t+1) = A'x$$

$$y = (A+B)x'$$

Present State		Input	Next State		Output
A	B	x	A	B	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

Also note alternate form of the State Table:
 Table 5.3 in text

Artwork
 © 2002 Prentice Hall, Inc.
 M. Morris Mano
 DIGITAL DESIGN, 3e.

State Diagram

cs309

Present State		Input x	Next State		Output y
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

 


Fig. 5-16 State Diagram of the Circuit of Fig. 5-15

Artwork
© 2002 Prentice Hall, Inc.
M. Morris Mano
DIGITAL DESIGN, 3e.

G. W. Cox – Spring 2010

State Diagram

cs309

Present State		Input x	Next State		Output y
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

 


Fig. 5-16 State Diagram of the Circuit of Fig. 5-15


Artwork
© 2002 Prentice Hall, Inc.
M. Morris Mano
DIGITAL DESIGN, 3e.

G. W. Cox – Spring 2010

Sequential circuit analysis (continued)

G. W. Cox – Spring 2010

Another D-FF example

 

$$D = x \text{ XOR } y \text{ XOR } A$$

 


Fig. 5-17 Sequential Circuit with D Flip-Flop


Note that since the circuit output is the state, we do not need to show the output value on the transition lines.

G. W. Cox – Spring 2010

Artwork
© 2002 Prentice Hall, Inc.
M. Morris Mano
DIGITAL DESIGN, 3e.

JK-FF Example

cs309

 

Input eqns:

$$J_A = B$$

$$K_A = x'B$$

$$J_B = x'$$

$$K_B = x \text{ XOR } A$$

Fig. 5-18 Sequential Circuit with JK Flip-Flop

G. W. Cox – Spring 2010

Artwork
© 2002 Prentice Hall, Inc.
M. Morris Mano
DIGITAL DESIGN, 3e.

JK-FF Example (2)

cs309

Input eqns:

$$J_A = B$$

$$K_A = x'B$$

$$J_B = x'$$

$$K_B = x \text{ XOR } A$$

Present State		Input	Next State		FF Inputs			
A	B	x	A	B	J _A	K _A	J _B	K _B
0	0	0	0	0	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	0	1	1	1	1	0
0	1	1	0	1	1	0	0	1
1	0	0	1	0	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	1	1	1	1	1	1
1	1	1	1	1	1	0	0	0

G. W. Cox – Spring 2010

JK-FF Example (3)

cs309

Input eqns:

$$\begin{aligned} J_A &= B \\ K_A &= x'B \\ J_B &= x' \\ K_B &= x \text{ XOR } A \end{aligned}$$

Characteristic Table

J	K	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	Q'(t)

"Reset"
"Set"
"Complement"

Present State		Input	Next State		FF Inputs			
A	B	x	A	B	J _A	K _A	J _B	K _B
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	1	0	0	0

G. W. Cox - Spring 2010

JK-FF Example (3)

cs309

Present State		Input	Next State		FF Inputs			
A	B	x	A	B	J _A	K _A	J _B	K _B
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	1	0	0	0

 


Fig. 5-19 State Diagram of the Circuit of Fig. 5-18

G. W. Cox - Spring 2010

Artwork
© 2002 Prentice Hall, Inc.
M. Morris Mano
DIGITAL DESIGN, 3e.

T-FF Example

cs309

 


Fig. 5-20 Sequential Circuit with T Flip-Flops

G. W. Cox - Spring 2010

Artwork
© 2002 Prentice Hall, Inc.
M. Morris Mano
DIGITAL DESIGN, 3e.

Mealy and Moore Designs

cs309

 


Fig. 5-16 State Diagram of the Circuit of Fig. 5-15

G. W. Cox - Spring 2010

Artwork
© 2002 Prentice Hall, Inc.
M. Morris Mano
DIGITAL DESIGN, 3e.

Mealy and Moore Designs

cs309

Moore Machine


 
 


Fig. 5-19 State Diagram of the Circuit of Fig. 5-18

 

(b) State diagram

Artwork
© 2002 Prentice Hall, Inc.
M. Morris Mano
DIGITAL DESIGN, 3e.

G. W. Cox – Spring 2010

cs309

Sequential Circuit Synthesis

G. W. Cox – Spring 2010

Synthesis procedure

cs309

1. Draw the state diagram
2. Assign binary codes to the states
3. Build the state table
4. Decide on FF types and write the FF input equations
5. Draw the logic diagram

G. W. Cox – Spring 2010

“111...” sequence detector

cs309

Design a circuit that detects a sequence of 3 or more consecutive 1's

 


Fig. 5-24 State Diagram for Sequence Detector

G. W. Cox – Spring 2010

Artwork
© 2002 Prentice Hall, Inc.
M. Morris Mano
DIGITAL DESIGN, 3e.

Assign binary codes to the states

cs309

 


Fig. 5-24 State Diagram for Sequence Detector

	A	B
S0	0	0
S1	0	1
S2	1	0
S3	1	1

Note that there are other ways to make this assignment

G. W. Cox – Spring 2010

Artwork
© 2002 Prentice Hall, Inc.
M. Morris Mano
DIGITAL DESIGN, 3e.

Build the state table

cs309

 


Fig. 5-24 State Diagram for Sequence Detector

	A	B
S0	0	0
S1	0	1
S2	1	0
S3	1	1

Present State		Input	Next State		Output
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	1	1	1	1

G. W. Cox – Spring 2010

Artwork
© 2002 Prentice Hall, Inc.
M. Morris Mano
DIGITAL DESIGN, 3e.

Determine FF Types and write the FF input equations

cs309

Say we use D-FF's

 


Fig. 5-25 Maps for Sequence Detector

G. W. Cox - Spring 2010

Artwork
© 2002 Prentice Hall, Inc.
M. Morris Mano
DIGITAL DESIGN, 3e.

Draw the logic diagram

cs309

$$D_A = Ax + Bx$$

$$D_B = Ax + B'x$$

$$y = AB$$

 


Fig. 5-26 Logic Diagram of Sequence Detector

G. W. Cox - Spring 2010

Artwork
© 2002 Prentice Hall, Inc.
M. Morris Mano
DIGITAL DESIGN, 3e.

Making it easier to develop FF Input Equations

cs309

The "Excitation Table"

D-FF			JK-FF				T-FF		
Q(t)	Q(t+1)	D	Q(t)	Q(t+1)	J	K	Q(t)	Q(t+1)	T
0	0	0	0	0	0	d	0	0	0
0	1	1	0	1	1	d	0	1	1
1	0	0	1	0	d	1	1	0	1
1	1	1	1	1	d	0	1	1	0

KNOW THESE!

G. W. Cox – Spring 2010

A JK-FF Example (1)

cs309

State Table

Present State		Input x	Next State	
A	B		A	B
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	1	1
1	1	0	1	1
1	1	1	0	0

G. W. Cox – Spring 2010

A JK-FF Example (2)

cs309

State Table			JK Excitation Table			
Present State		Input	Next State		Q(t)	Q(t+1)
A	B	x	A	B	J	K
0	0	0	0	0	0	d
0	0	1	0	1	0	1
0	1	0	1	0	1	d
0	1	1	0	1	d	1
1	0	0	1	0	1	0
1	0	1	1	1	d	0
1	1	0	1	1	d	0
1	1	1	0	0	d	0

State Table with FF Inputs							
Present State		Input	Next State		FF Inputs		
A	B	x	A	B	JA	KA	JB
0	0	0	0	0	0	d	d
0	0	1	0	1	0	d	1
0	1	0	1	0	1	d	d
0	1	1	0	1	0	d	d
1	0	0	1	0	d	0	d
1	0	1	1	1	d	0	1
1	1	0	1	1	d	0	d
1	1	1	0	0	d	1	d

G. W. Cox – Spring 2010

A JK-FF Example (3)

cs309

Present State		Input	Next State		FF Inputs			
A	B	x	A	B	JA	KA	JB	KB
0	0	0	0	0	0	d	0	d
0	0	1	0	1	0	d	1	d
0	1	0	1	0	1	d	d	1
0	1	1	0	1	0	d	d	0
1	0	0	1	0	d	0	0	d
1	0	1	1	1	d	0	1	d
1	1	0	1	1	d	0	d	0
1	1	1	0	0	d	1	d	1

 


Fig. 5-27 Maps for J and K Input Equations

G. W. Cox – Spring 2010

Artwork
© 2002 Prentice Hall, Inc.
M. Morris Mano
DIGITAL DESIGN, 3e.

A JK-FF example (4)

cs309

$$\begin{aligned} J_A &= Bx' \\ K_A &= Bx \\ J_B &= x \\ K_B &= (A \text{ XOR } x)' \end{aligned}$$

 


Fig. 5-28 Logic Diagram for Sequential Circuit with JK Flip-Flops

G. W. Cox – Spring 2010

cs309

A simple binary counter

G. W. Cox – Spring 2010

State diagram, state table, FF inputs

cs309

 


Fig. 5-29 State Diagram of 3-Bit Binary Counter
© 2002 Prentice Hall, Inc.
M. Morris Mano
DIGITAL DESIGN, 3e.

For T Flip Flops

PS			NS			FF inputs		
A_2	A_1	A_0	A_2	A_1	A_0	T_{A2}	T_{A1}	T_{A0}
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

Use K-Maps to determine:

$$T_{A2} = A_1 A_0$$

$$T_{A1} = A_0$$

$$T_{A0} = 1$$

G. W. Cox – Spring 2010

Circuit

cs309

 


Fig. 5-31 Logic Diagram of 3-Bit Binary Counter

© 2002 Prentice Hall, Inc.
M. Morris Mano
DIGITAL DESIGN, 3e.

G. W. Cox – Spring 2010